

**0539****Code : 9EC-51**Register  
Number

				9	0	2	6
--	--	--	--	---	---	---	---

**V Semester Diploma Examination May, 2012****E & C BOARD****INDUSTRIAL AUTOMATION****Time : 3 Hours ]****[ Max. Marks : 100**

- Instructions :** (1) Section – I is compulsory.  
(2) Answer any **two** main questions from each of the remaining sections.

**SECTION – I**

1. (a) Fill in the blanks : 5  
(i) IGBT is a \_\_\_\_\_ controlled device.  
(ii) Average value of output voltage of SCR can be controlled by controlling the \_\_\_\_\_.  
(iii) Step-up chopper operates in \_\_\_\_\_ quadrant.  
(iv) \_\_\_\_\_ commutation does not need any external circuitry.  
(v) PID stands for \_\_\_\_\_.  
(b) Sketch & explain the structure and characteristics of GTO. 5

**SECTION – II**

2. (a) With neat structural diagram explain the characteristics of IGBT. 8  
(b) Explain the working principle of Reverse recovery diode. 4  
(c) List the classification of power semiconductor diodes. 3
3. (a) Explain the working principle of triac with neat circuit diagram. 6  
(b) Explain how SCR can be triggered using UJT relaxation Oscillator. 5  
(c) Explain auxiliary commutation using neat diagram. 4
4. (a) Explain single phase fullwave mid point controlled rectifier with neat circuit and waveform. 8  
(b) Explain light dimmer circuit using diac with neat circuit. 7

**[Turn over**

## SECTION – III

5. (a) Define chopper and give its classification. 4  
(b) Explain two quadrant class D chopper. 6  
(c) Explain briefly the control schemes of chopper. 5
6. (a) Explain the working principle of basic series inverter. 7  
(b) Explain the operation of dual converter circuit. 5  
(c) Explain single PWM with waveform. 3
7. (a) Explain speed control of DC motor using field control method. 8  
(b) Explain over voltage protection of motor. 4  
(c) List the advantages of electronic control of motor. 3

## SECTION – IV

8. (a) With the help of block diagram, explain the PLC System. 6  
(b) Explain briefly PLC Scanning. 3  
(c) List the advantages of PLC over relay logic. 6
9. (a) Explain OR gate and its PLC logic equivalent. 5  
(b) Explain briefly input and output register. 5  
(c) Explain PLC counter with an example. 5
10. (a) Brief out move and basic number comparison functions with an example. 5  
(b) Explain the necessity of PID in process control and explain its principle of operation with neat diagram. 6  
(c) Explain PID module with block diagram. 4
-

**0548****Code : 9EC-51**Register  
Number

1	1	9	E	C	0	9057
---	---	---	---	---	---	------

**V Semester Diploma Examination, November 2011****E & C BOARD****INDUSTRIAL AUTOMATION****Time : 3 Hours ]****[ Max. Marks : 100**

- Instructions :** (1) Section – I is *compulsory*.  
(2) Answer **six** full questions choosing any **two** full questions each from Section – II, III and IV.

**SECTION – I**

1. (a) Fill in the blanks : 5  
(i) A UJT after reaching valley point goes into \_\_\_\_\_ state.  
(ii) An SCR will be turned off using \_\_\_\_\_ circuit.  
(iii) Step up chopper operates in \_\_\_\_\_ quadrant  
(iv) PLC stands for \_\_\_\_\_  
(v) \_\_\_\_\_ register holds the contents of calculation on PLC.
- (b) What is a cycloconverter ? List its application. 5

**SECTION – II**

2. (a) Explain the working principle of SCR. 6  
(b) Mention the advantages of Triac over SCR. 3  
(c) List Turn on methods of an SCR and explain any one of them. 6
3. (a) Briefly explain the working and VI characteristic of Diac. 6  
(b) Explain the following terms : 6  
(i) Natural commutation  
(ii) Forced commutation  
(iii) Resonant commutation  
(c) Write the neat circuit diagram of SCR being triggered by UJT. 3
4. (a) Explain three phase full wave controlled rectifier circuit along with input and output waveforms. 10  
(b) Explain variable DC link inverter with block diagram. 5

**[Turn over**

## SECTION - III

5. (a) Classify the inverters based on commutation and explain. 5  
 (b) Explain the principle of operation of single phase to single phase cycloconverter. Draw the required waveforms also. 10
6. (a) Explain the basic principle of chopper operations. 7  
 (b) Explain the operation of two quadrant DC choppers. 4  
 (c) Explain briefly PWM technique used in inverters. 4
7. (a) List the advantages of electronic control of electric devices. 4  
 (b) Explain over voltage protection of DC motors. 3  
 (c) With neat block diagram explain the field control method for speed control of DC motor. 8

## SECTION - IV

8. (a) List the type of counters used in PLC and explain. Write the relative diagrams. 9  
 (b) With neat block diagram explain PID module used in PLC. 6
9. (a) With relevant diagram explain the jump functions used in PLC programming. 7  
 (b) List the timer types used in PLC and explain each of them with neat diagram. 8
10. (a) Explain in detail with relevant diagrams the move functions used in PLC programming. 6  
 (b) With neat diagram show and explain general levels of control of an industry used in PLC networking. 9