

Basic Electrical Engineering



Q.P. Code :803301

(3 Hours)

[Total Marks : 80


- N.B. :** (1) Question No.1 is compulsory.
 (2) Answer any **THREE** questions from remaining five questions.
 (3) **Figures** to right indicate **full** marks.
 (4) Assume suitable data if required.

1. A) State Maximum Power Transfer Theorem 2
 B) Derive the formula to convert a delta circuit into an equivalent star 4
 C) Define Average value and RMS value of an alternating quantity 4
 D) Prove that power in a 3-phase delta connected system is 3 times that of a star connected system. 4
 E) Explain the working principle of a single phase transformer. 4
 F) What is the use of commutator in a DC machine. 2
2. A) Obtain current through $1\ \Omega$ resistance by using Super position theorem, in fig 2.A. 10




- B) A coil is connected across a non-inductive resistance of $120\ \Omega$. When a $240\ \text{V}$, $50\ \text{Hz}$ supply is applied to this circuit the coil draws a current $5\ \text{A}$ and total current is $6\ \text{A}$. Determine the power and power factor of
 i) the coil
 ii) the whole circuit

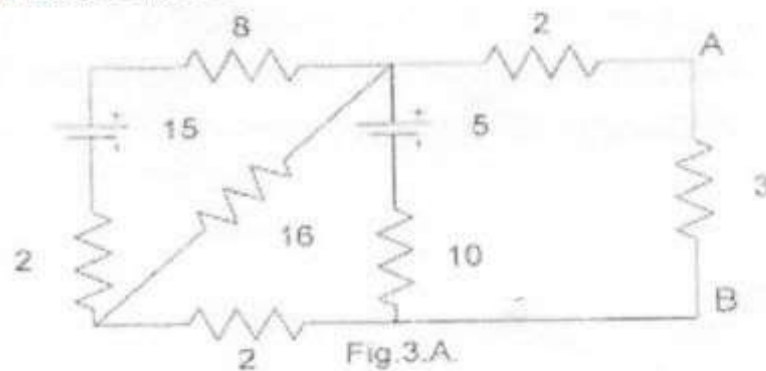3. A) Obtain Norton's equivalent circuit of the network shown in fig. 3.A, across the terminals A and B 10




[TURN OVER]

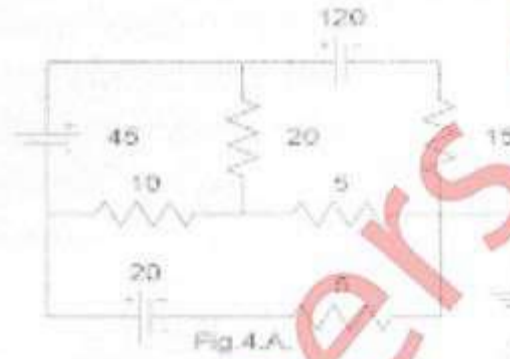- B) A series RLC circuit, if ω_0 is the resonant frequency, ω_1 and ω_2 are the half power frequencies, prove that $\omega_0 = \sqrt{\omega_1 \omega_2}$ 5
- C) Derive the equivalent circuit of a 1-phase transformer. 5
4. A) Obtain current through 15Ω resistance by nodal analysis in fig.4.A. Take reference node as marked. 10



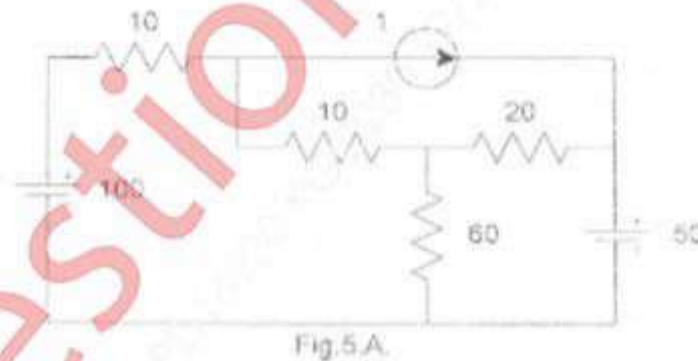- B) In a balanced 3 phase, star connected system, a wattmeter is connected with its current coil in series with Y line and pressure coil between Y and R lines. Draw a neat circuit diagram showing the above wattmeter connection. Assuming a lagging power factor, draw the corresponding phasor diagram and derive the wattmeter reading in terms of line voltage, line current and phase angle. 10
5. A) Obtain current through 60Ω resistance by Mesh analysis in fig.5.A. 6



- B) Develop the phasor diagram of a single transformer supplying to a resistive load. 8
- C) Derive the emf equation of a DC generator. 6
6. A) A resistor and a pure reactance are connected in series across a 150 V ac supply. When the frequency is 40 Hz, the circuit draws 5 A. When the frequency is increased to 50 Hz, the circuit draws 6 A. Find the value of resistance and the element value of the reactance. Also find the power drawn in the second case. 10

B) A single phase 10 KVA, 500 V/250 V, 50 Hz transformer has the following 10 constants.

Resistance : primary = 0.2 ohms, secondary = 0.5 ohms

Reactance : primary = 0.4 ohms, secondary = 0.1 ohms

Resistance of equivalent exciting circuit w.r.t. primary = 1500 ohms

Reactance of equivalent exciting circuit w.r.t. primary = 750 ohms

What will be the reading of the instruments placed in primary side when the transformer is connected for OC and SC tests ?
