

Note: 1) Question no. 1 is compulsory.


- 2) Solve any three questions out of remaining.
- 3) Fig. to the right indicates maximum marks.
- 4) Assume suitable data wherever necessary but justify the same.




Q1. Solve any five.

(5x4 = 20)

 - a) Determine the value of R_c such that $V_c = 5V$ and $\beta = 50$.



 - b) State and explain Miller's Theorem.
- c) Design a self bias circuit using JFET for $I_D = 3mA$, $V_{DD} = 20V$ and $V_{DS} = 0.6 V_{DD}$.
($I_{DSS} = 8mA$, $V_P = -4V$)
- d) Explain various types of capacitors.
- e) Determine the values of coupling capacitors C_{C1} and C_{C2} if $r_{\pi} = 1.5K\Omega$, $\beta = 120$ and $f_L = 20Hz$.




- f) Explain concept of zero temperature drift in JFET.

[TURN OVER

Q2. A) Calculate 1) I_{BQ} , I_{CQ} 2) g_m , r_{π} 3) Small signal voltage gain 10

For the circuit given below.

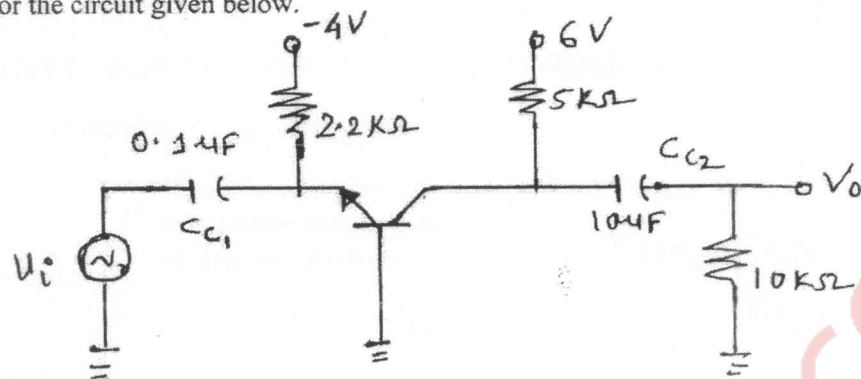


Take $\beta = 110$

Q2 B) Explain the concept of LC filter in power supply circuit and hence derive expression for ripple factor of LC filter. 10

Q3 A) Explain concept of shunt Zener regulator. For a shunt Zener regulator giving output voltage of 10 V and load resistance varying from $5k\Omega$ to $10k\Omega$, V_{in} is varying between 18V to 22V. Find R_s , P_{zmax} , S_v and R_o . Assume $R_z = 4\Omega$ and $I_{zmin} = 50\mu A$.

 B) Determine I_{DQ} , V_{GSQ} , V_{DSQ} if $I_{DSS} = 9mA$ and $V_p = -3V$ for the circuit given below. 10



Take $R_s = 1.5 k\Omega$

Q4 A) Design capacitive filter with FWR using two diodes with ripple factor less than 5%. 10

Output voltage is 24V and load current 200mA. The input line voltage of 230V/ 50Hz is available.

B) Determine the values of biasing components for a CE configuration if $V_{CC} = 12V$, $V_{CE} = 6V$, $R_C = 1k\Omega$, $V_{BE} = 0.6V$, $\beta = 180$ for the following circuit. 10

- i) Fixed bias without R_E
- ii) Voltage Divider bias with $V_{RE} = 10\%$ of V_{CC} and $S_1 = 8$

[TURN OVER

Q5 A) For JFET if $I_{DSS} = 6 \text{ mA}$, $V_P = -6\text{V}$ $r_d = \infty$, $C_{gd} = 4\text{pF}$, $C_{gs} = 6\text{pF}$, $C_{ds} = 1\text{pF}$ 15


Determine i) V_{GSQ} ii) I_{DQ}

iii) g_{mo} iv) g_m

v) Midband voltage gain A_v

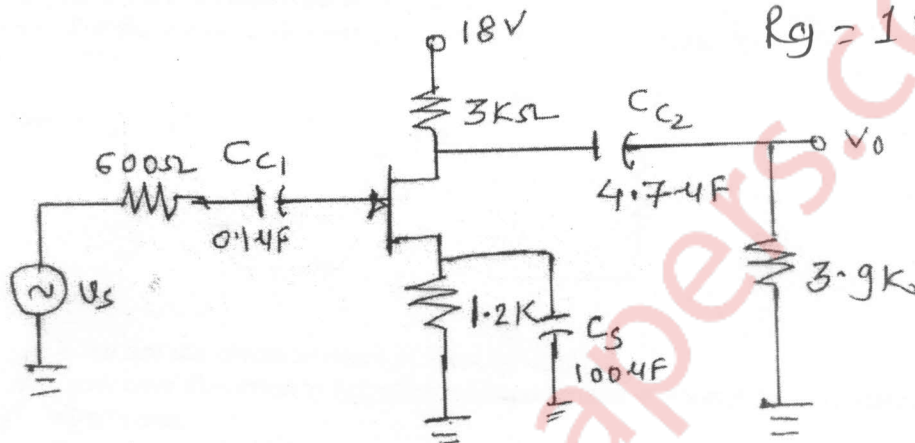vi) Higher cut off frequency

Take Gate resistance
 $R_g = 1 \text{ M}\Omega$



B) Explain high frequency \square equivalent model of common emitter BJT. 5

Q6. Design single stage CS amplifier using mid-point biasing method for voltage gain of 12, 20

$F_L = 20 \text{ Hz}$, $R_L = 10\text{K}\Omega$, $V_o = 3.5\text{V}$

(Use JFET parameters $I_{DSS} = 7\text{mA}$, $V_P = -2.5\text{V}$, $g_{mo} = 5600\mu\text{S}$, $r_d = 50\text{K}\Omega$)